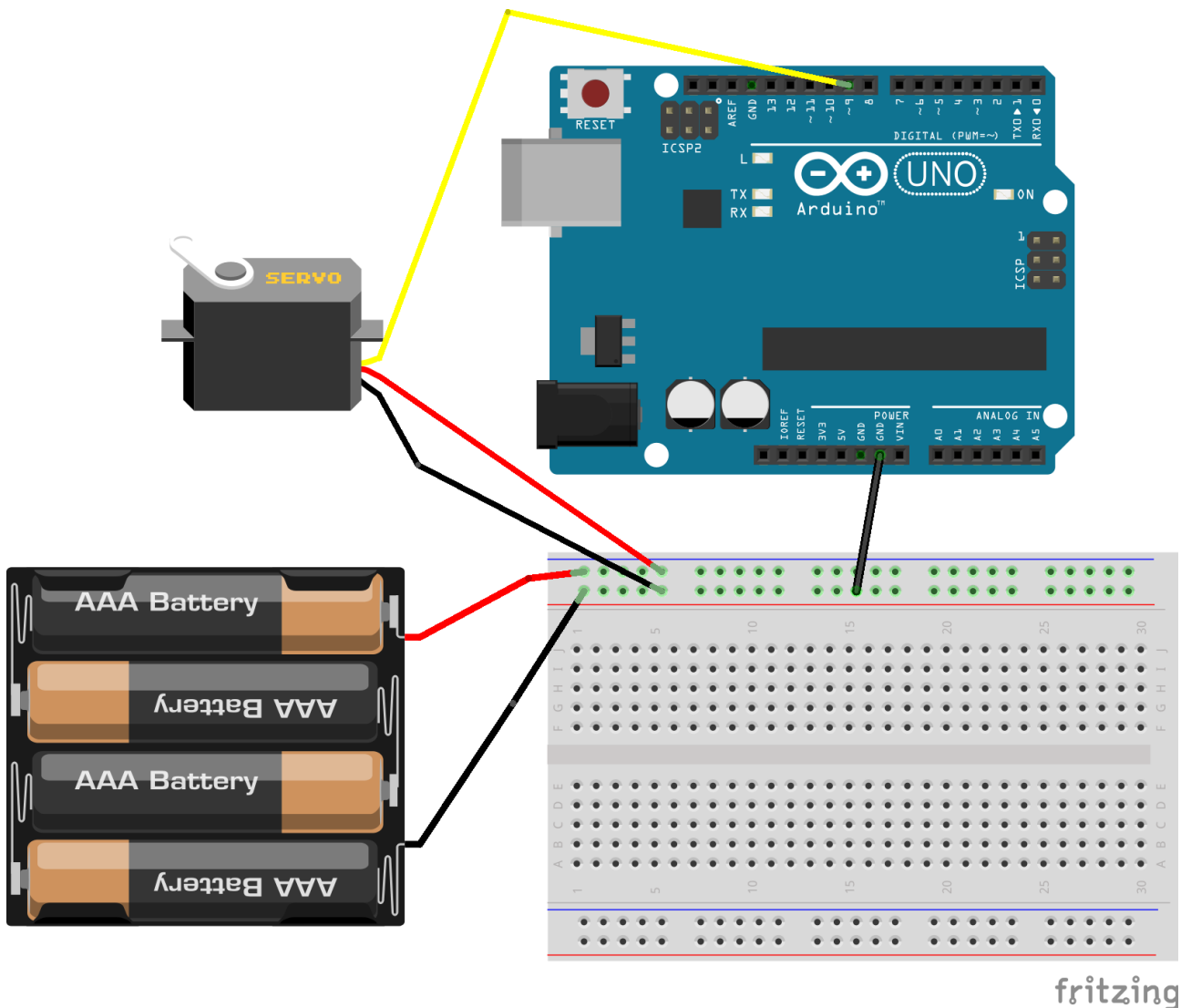


Circuit 3 - Servo motor control

For this circuit you simply need to make the following connections between the Arduino components.

Notes:

- The three wires may be different colours to the colours pictured in the diagram. As a general rule, White/Yellow is always the signal wire, Brown/Black is the Ground, and Red/Orange is the



*Note.

Some servos you may be able to power directly off the output pins, however these will only ever be very small and weak servos.